Useless Notes for November 13, 2007

Basic Math that I Should Know Already but Don't

1.
$$(a+\jmath b)^* = (a-\jmath b)$$

Maximum Power Transfer

Chapter 5

- 1. $V_{rms} = \frac{V_M}{sqrt2}$ for a sinusoid.
- 2. $I_{rms} = \frac{I_M}{sqrt2}$ for a sinusoid.
- 3. $P_{ave} = \frac{V_M I_M}{2}$

Complex Power

Chapter 11

- 1. $\Sigma P_{supplied} = \Sigma P_{absorbed}$
- 2. $S = \frac{VI^*}{2} = \frac{V_m I_m}{2} \angle (\theta_v \theta_i)$