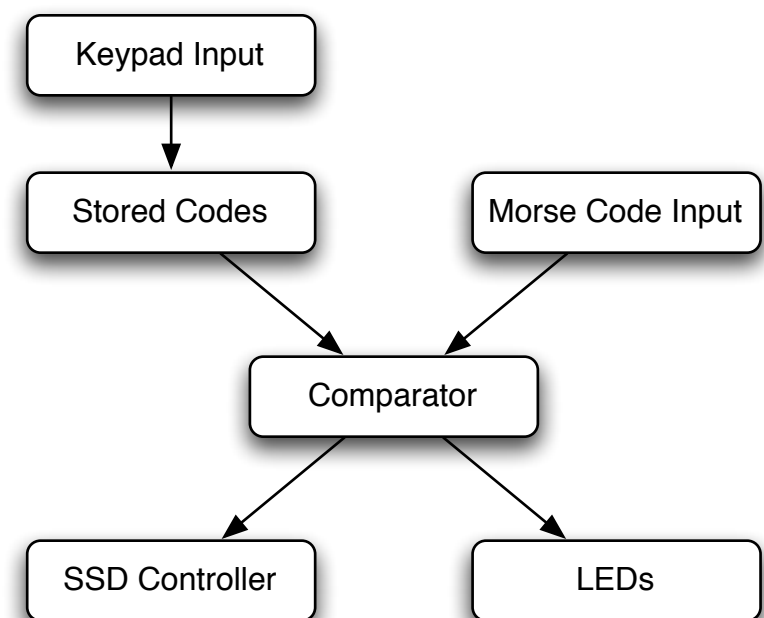


ECE 2220 Final Design Project

Burke Libbey
John Ermitanio
Crystal Kotlar

The Project

- Monitor NDB transmission
- Compare transmitted morse code with stored sequence
- Raise error if sequences don't match



Inputs


- Keypad selects sequence to monitor
- Pushbutton sends sequence

Outputs

- SSD shows sequence being monitored or Error
- Red LED: Error
- Yellow LED: Transmitting
- Green LED: Successful Transmission


Selector

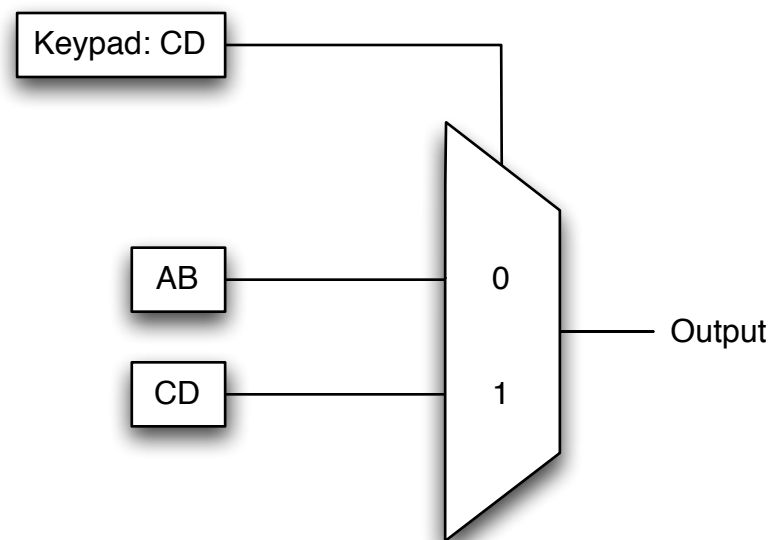- By default, AB is passed through, unless Keypad:CD has been pressed




Comparator

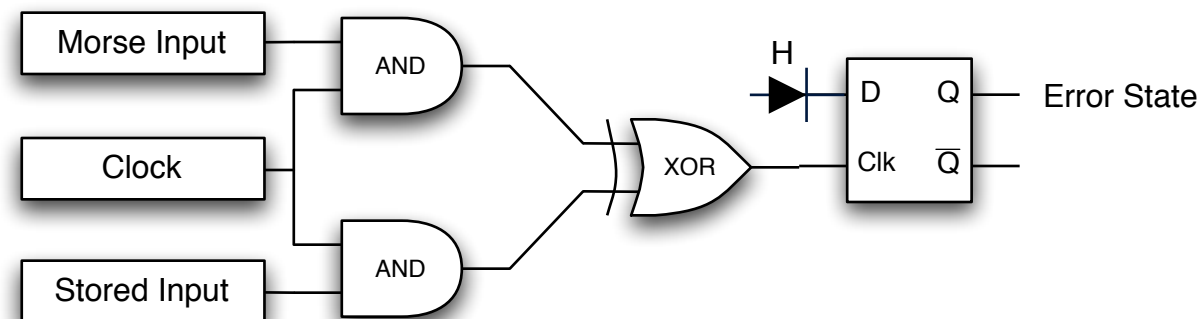- Uses an XOR to compare Input and stored sequence
- Triggers a DFF on first error




Zero-overflow Detection

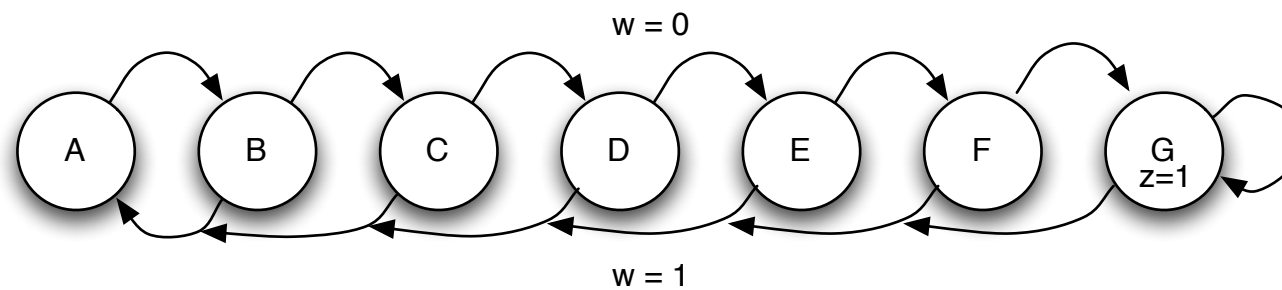- Outputs 1 when 7 sequential zeroes are encountered




Seven Segment Displays

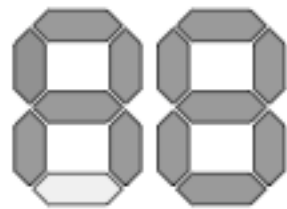
- 'AB' or 'CD' when listening for a sequence or finished listening successfully.
- 'EE' when transmission failed



(a) AB

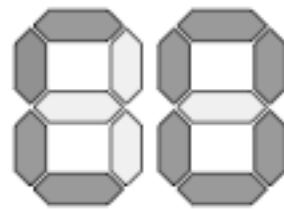

(b) CD

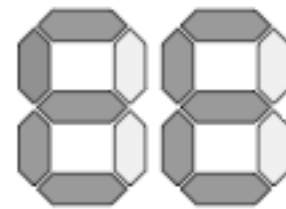

(c) EE

Interesting Features

- Comparator uses negative clock edge

Questions?